

# Chapter 4

## The Building Blocks: Binary Numbers, Boolean Logic, and Gates



**INVITATION TO  
Computer Science**

**6<sup>TH</sup>  
EDITION**

# Objectives

After studying this chapter, students will be able to:

- Translate between base-ten and base-two numbers, and represent negative numbers using both sign-magnitude and two's complement representations
- Explain how floating-point numbers, character, sounds, and images are represented inside the computer
- Build truth tables for Boolean expressions and determine when they are true or false
- Describe the relationship between Boolean logic and computer hardware/circuits



# Objectives (continued)

After studying this chapter, students will be able to:

- Construct circuits using the sum-of-products circuit design algorithm, and analyze simple circuits to determine their truth tables
- Explain how the compare-for-equality (CE) circuit works and its construction from one-bit CE circuits, and do the same for the adder circuit and its one-bit adder parts
- Describe the purpose and workings of multiplexor and decoder control circuits

# Introduction


- This chapter is about how computers work
- All computing devices are built on the ideas in this chapter
  - Laptops, desktops
  - Servers, supercomputers
  - Game systems, cell phones, MP3 players
  - Calculators, singing get-well cards
  - Embedded systems, in toys, cars, microwaves, etc.



# The Binary Numbering System

- How can an electronic (or magnetic) machine represent information?
- Key requirements: clear, unambiguous, reliable
- External representation is human-oriented
  - base-10 numbers
  - keyboard characters
- Internal representation is computer-oriented
  - base-2 numbers
  - base-2 codes for characters

**FIGURE 4.1**

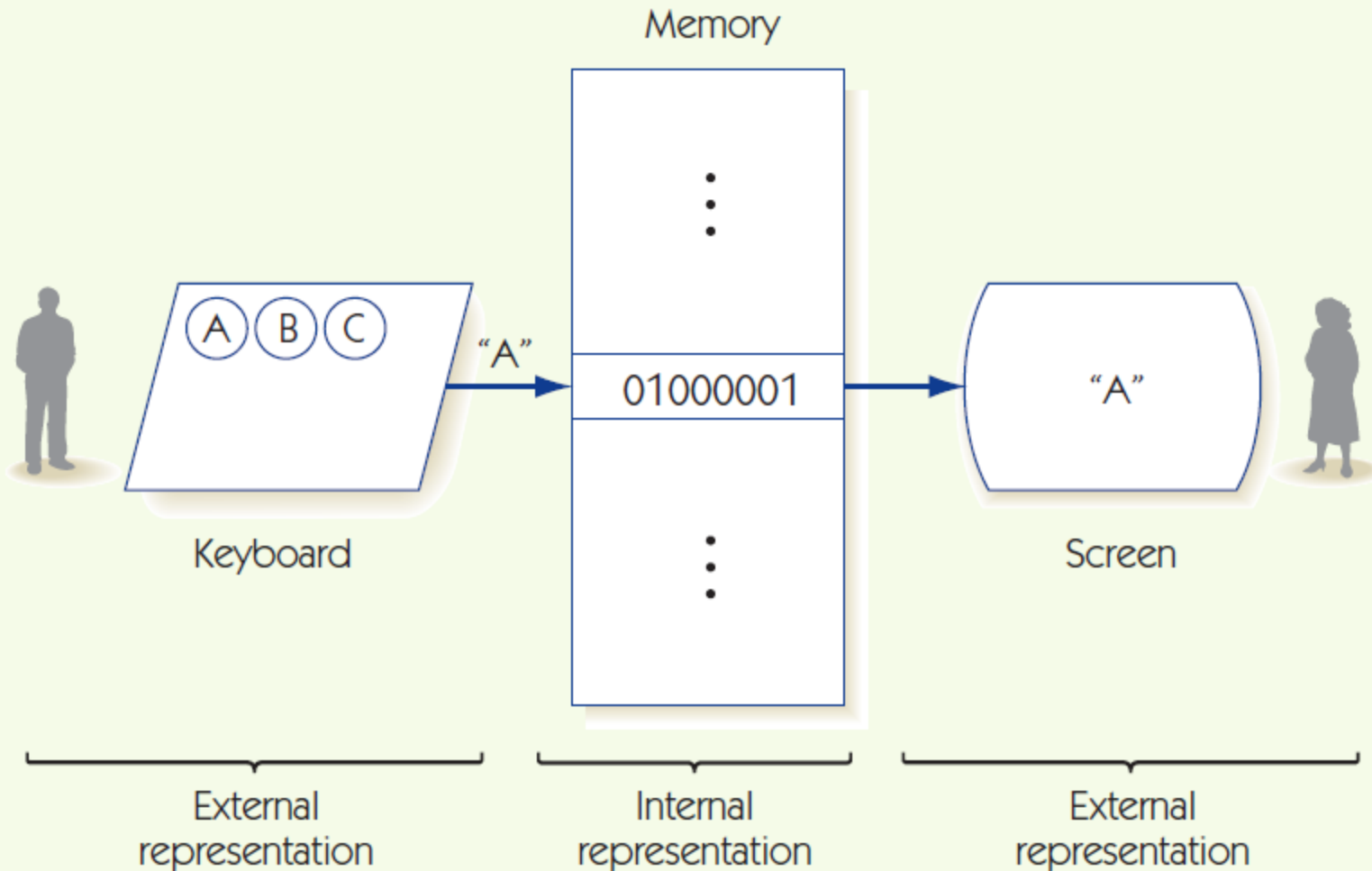

**Distinction between external and internal representation of information**



# The Binary Numbering System (continued)

- The **binary numbering system** is a base-2 **positional numbering system**
- Base ten:
  - Uses 10 digits: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9
  - Each place corresponds to a power of 10
  - $1,943 = 1 * 10^3 + 9 * 10^2 + 4 * 10^1 + 3 * 10^0$
- Base two:
  - Uses 2 digits: 0, 1
  - Each place corresponds to a power of 2
  - $1101 = 1 * 2^3 + 1 * 2^2 + 0 * 2^1 + 1 * 2^0 = 13$

**FIGURE 4.2**

| <b>Binary</b> | <b>Decimal</b> | <b>Binary</b> | <b>Decimal</b> |
|---------------|----------------|---------------|----------------|
| 0             | 0              | 10000         | 16             |
| 1             | 1              | 10001         | 17             |
| 10            | 2              | 10010         | 18             |
| 11            | 3              | 10011         | 19             |
| 100           | 4              | 10100         | 20             |
| 101           | 5              | 10101         | 21             |
| 110           | 6              | 10110         | 22             |
| 111           | 7              | 10111         | 23             |
| 1000          | 8              | 11000         | 24             |
| 1001          | 9              | 11001         | 25             |
| 1010          | 10             | 11010         | 26             |
| 1011          | 11             | 11011         | 27             |
| 1100          | 12             | 11100         | 28             |
| 1101          | 13             | 11101         | 29             |
| 1110          | 14             | 11110         | 30             |
| 1111          | 15             | 11111         | 31             |

Binary-to-decimal conversion table



# The Binary Numbering System (continued)

- Converting from binary to decimal
  - Add up powers of two where a 1 appears in the binary number
- Converting from decimal to binary
  - Repeatedly divide by two and record the remainder
  - Example, convert 9:
    - $9/2 = 4$  remainder 1, binary number = 1
    - $4/2 = 2$  remainder 0, binary number = 01
    - $2/2 = 1$  remainder 0, binary number = 001
    - $1/2 = 0$  remainder 1, binary number = 1001

# The Binary Numbering System (continued)

- Computers use fixed-length binary numbers for integers, e.g., with 4 bits could represent 0 to 15
- **Arithmetic overflow:** when computer tries to make a number that is too large, e.g.  $14 + 2$  with 4 bits
- Binary addition:  $0+0=0$ ,  $0+1=1$ ,  $1+0=1$ ,  $1+1=0$  with carry of 1
- Example:  $0101 + 0011 = 1000$



# The Binary Numbering System (continued)

- Signed integers include negative numbers
- **Sign/magnitude notation** uses 1 bit for sign, the rest for value
  - $+5 = 0101$ ,  $-5 = 1101$
  - $0 = 0000$  and  $1000!$
- **Two's complement representation**: to make the negative of a number, flip every bit and add one
  - $+5 = 0101$ ,  $-5 = 1010 + 1 = 1011$
  - $0 = 0000$ ,  $-0 = 1111 + 1 = 0000$

# The Binary Numbering System (continued)


- Floating point numbers use binary scientific notation
  - **Scientific notation**, base 10:  $1.35 \times 10^{-5}$
  - Base 2:  $3.25_{10} = 11.01_2 = 1.101 \times 2^1$
- Characters and text: map characters onto binary numbers in a standard way
  - ASCII (8-bit numbers for each character)
  - Unicode (16-bit numbers for each character)

# The Binary Numbering System (continued)

- Sounds and images require converting naturally **analog representations to digital representations**
- Sound waves characterized by:
  - **amplitude**: height of the wave at a moment in time
  - **period**: length of time until wave pattern repeats
  - **frequency**: number of periods per time unit



**FIGURE 4.4**

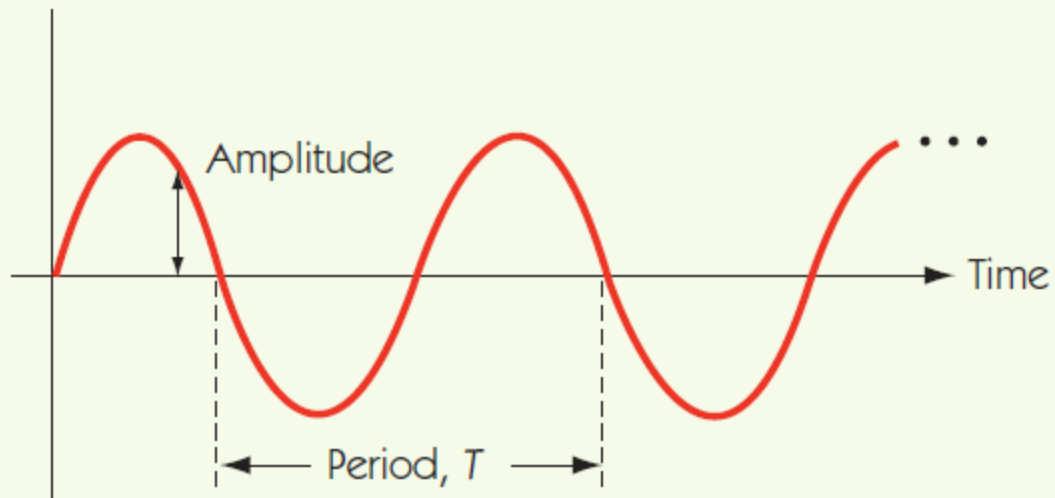


Example of sound represented as a waveform


# The Binary Numbering System (continued)

- **Digitize:** to convert to a digital form
- **Sampling:** record sound wave values at fixed, discrete intervals
- To reproduce sound, approximate using samples
- Quality determine by:
  - **Sampling rate:** number of samples per second
    - More samples = more accurate wave form
  - **Bit depth:** number of bits per sample
    - More bits = more accurate amplitude

FIGURE 4.5

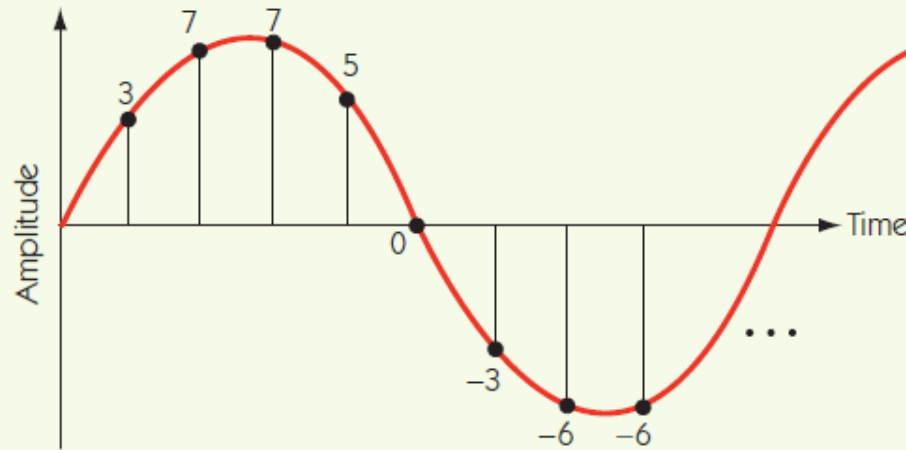

(a)

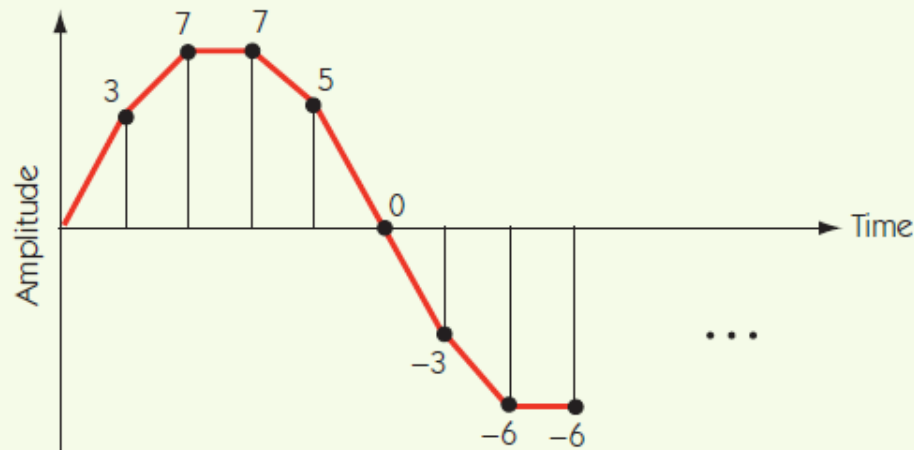

(b)

Digitization of an analog signal

(a) Sampling the original signal


(b) Recreating the signal from the sampled values

# The Binary Numbering System (continued)

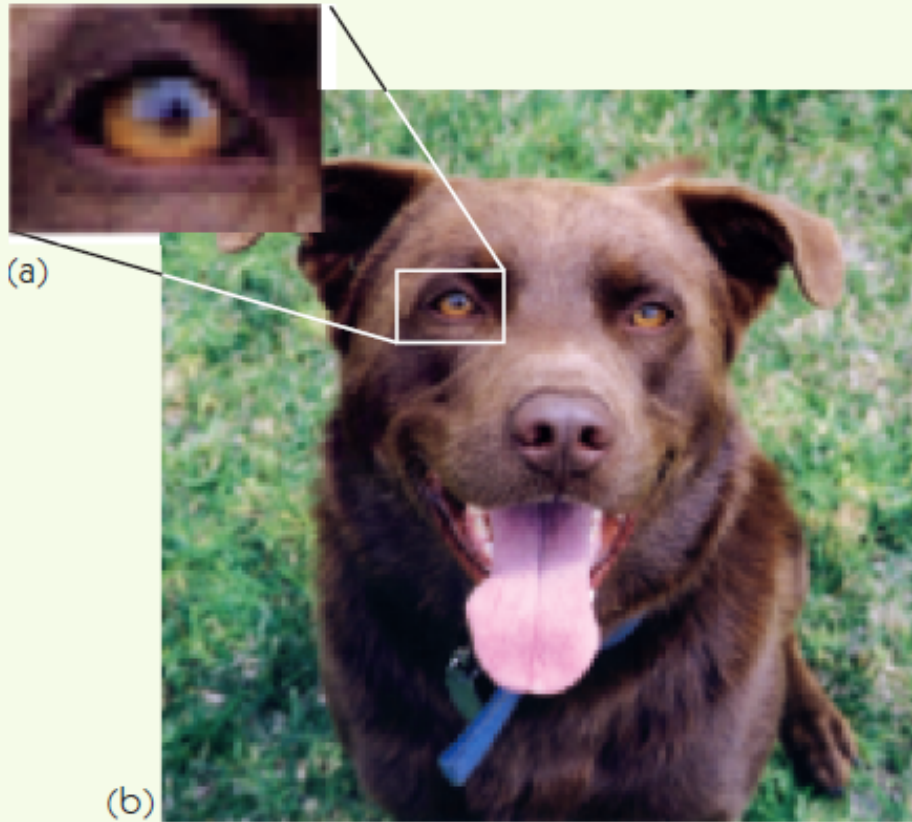- Image sampling: record color or intensity at fixed, discrete intervals in two dimensions
- Pixels: individual recorded samples
- **RGB encoding scheme:**
  - Colors are combinations of red, green, and blue
  - One byte each for red, green, and blue
- **Raster graphics** store picture as two-d grid of pixel values

 


**FIGURE 4.6**



Example of a digitized photograph  
(a) Individual pixels in the photograph  
(b) Photograph

**FIGURE 4.7**



An eight-level gray scale

# The Binary Numbering System (continued)

- Data size: how much to store:
  - 1000 integer values
  - 10-page text paper
  - 60-second sound file
  - 480 by 640 image
- **Data compression:** storing data in a reduced-size form to save space/time
  - Lossless: data can be perfectly restored
  - Lossy: data cannot be perfectly restored

**FIGURE 4.8**

| <b>Letter</b> | <b>4-bit Encoding</b> | <b>Variable Length Encoding</b> |
|---------------|-----------------------|---------------------------------|
| A             | 0000                  | 00                              |
| I             | 0001                  | 10                              |
| H             | 0010                  | 010                             |
| W             | 0011                  | 110                             |
| E             | 0100                  | 0110                            |
| O             | 0101                  | 0111                            |
| M             | 0110                  | 11100                           |
| K             | 0111                  | 11101                           |
| U             | 1000                  | 11110                           |
| N             | 1001                  | 111110                          |
| P             | 1010                  | 1111110                         |
| L             | 1011                  | 1111111                         |
|               | (a)                   | (b)                             |


Using variable-length code sets

- (a) Fixed length
- (b) Variable length


 
# The Binary Numbering System (continued)


- Computers use binary because “bistable” systems are reliable
  - current on/off
  - magnetic field left/right



# The Binary Numbering System (continued)


- **Transistors**
  - Solid-state switches
  - Change on/off when given power on control line
  - Extremely small (billions per chip)
  - Enable computers that work with **gigabytes** of data

FIGURE 4.11

 

Simplified model of a transistor

**FIGURE 4.10**

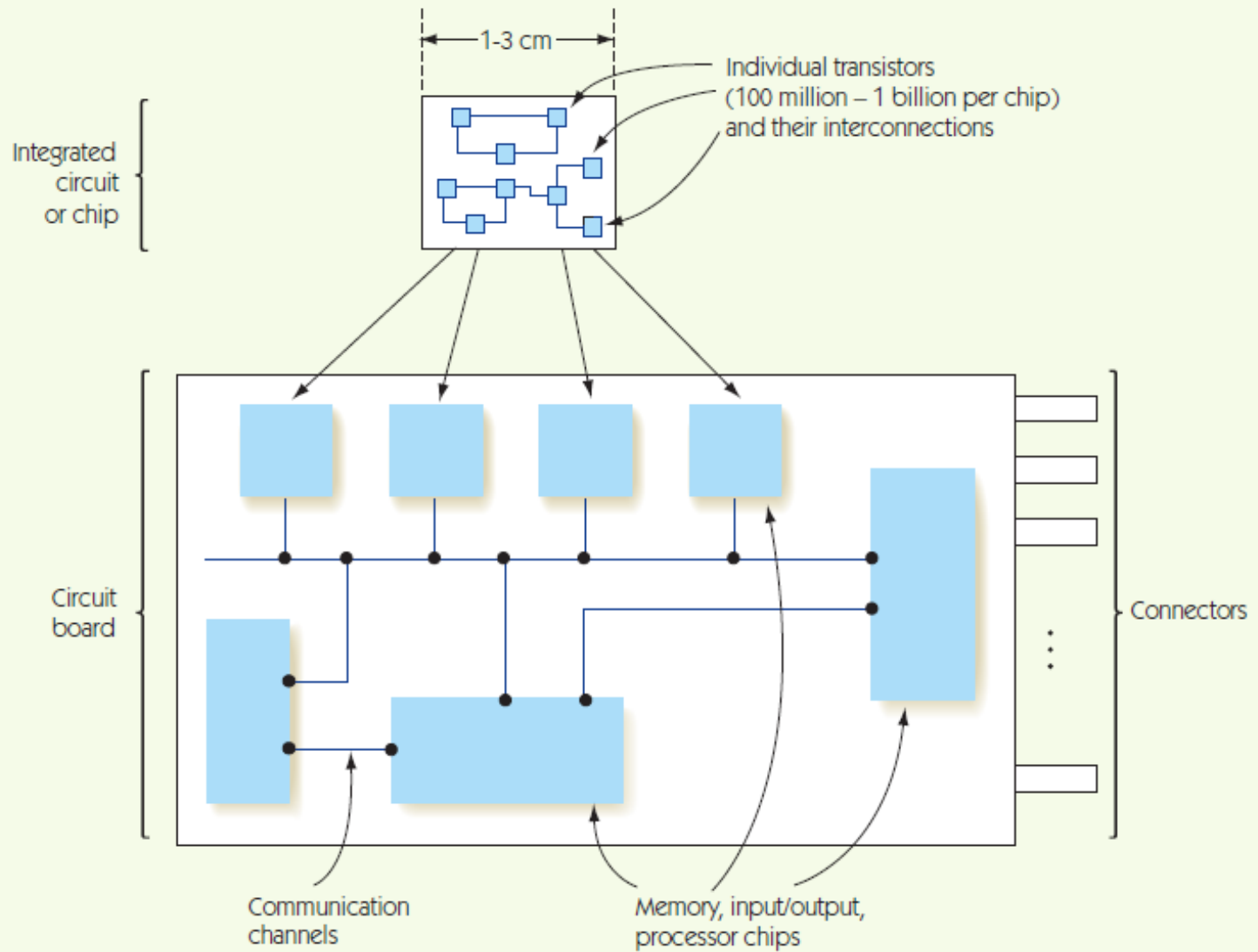

**Relationships among transistors, chips, and circuit boards**

# Boolean Logic and Gates

- **Boolean logic:** rules for manipulating true/false
- Boolean expressions can be converted to circuits
- **Hardware design/logic design** pertains to the design and construction of new circuits
- Note that 1/0 of binary representations maps to true/false of Boolean logic
- Boolean expressions:  $x \leq 35$ ,  $a = 12$
- Boolean operators:  $(0 \leq x)$  AND  $(x \leq 35)$ ,  $(a = 12)$  OR  $(a = 13)$ , NOT  $(a = 12)$   
 $(0 \leq x) \cdot (x \leq 35)$ ,  $(a = 12) + (a = 13)$ ,  $\sim(a = 12)$



# Boolean Logic and Gates (continued)

- **Truth tables** lay out true/false values for Boolean expressions, for each possible true/false input
- Example:  $(a \cdot b) + (a \cdot \sim b)$

| a     | b     | $\sim b$ | $(a \cdot b)$ | $(a \cdot \sim b)$ | $(a \cdot b) + (a \cdot \sim b)$ |
|-------|-------|----------|---------------|--------------------|----------------------------------|
| true  | true  | false    | true          | false              | true                             |
| true  | false | true     | false         | true               | true                             |
| false | true  | false    | false         | false              | false                            |
| false | false | true     | false         | false              | false                            |

**FIGURE 4.12**

| Inputs |       | Output<br>a AND b<br>(also written $a \cdot b$ ) |
|--------|-------|--|
| a      | b     |  |
| False  | False | False  |
| False  | True  | False  |
| True   | False | False  |
| True   | True  | True   |

Truth table for the AND operation

**FIGURE 4.13**

| Inputs |       | Output<br>a OR b<br>(also written $a + b$ ) |
|--------|-------|---|
| a      | b     |   |
| False  | False | False                                       |
| False  | True  | True  |
| True   | False | True  |
| True   | True  | True  |

Truth table for the OR operation


**FIGURE 4.14**

| Input | Output<br>NOT a<br>(also written $\bar{a}$ ) |
|-------|--|
| a     |  |
| False | True   |
| True  | False  |

Truth table for the NOT operation

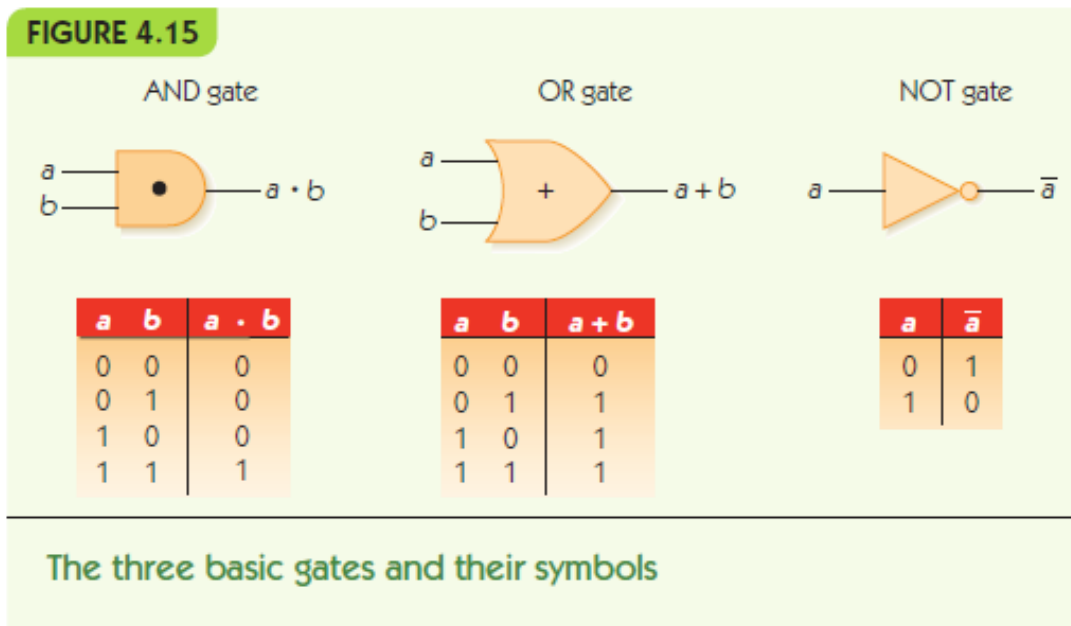
# Boolean Logic and Gates (continued)

- **Gate:** an electronic device that operates on inputs to produce outputs
- Each gate corresponds to a Boolean operator




# Boolean Logic and Gates (continued)

- Gates are built from transistors
- NOT gate: 1 transistor
- AND gate: 3 transistors
- OR gate: 3 transistors
- NAND and NOR: 2 transistors

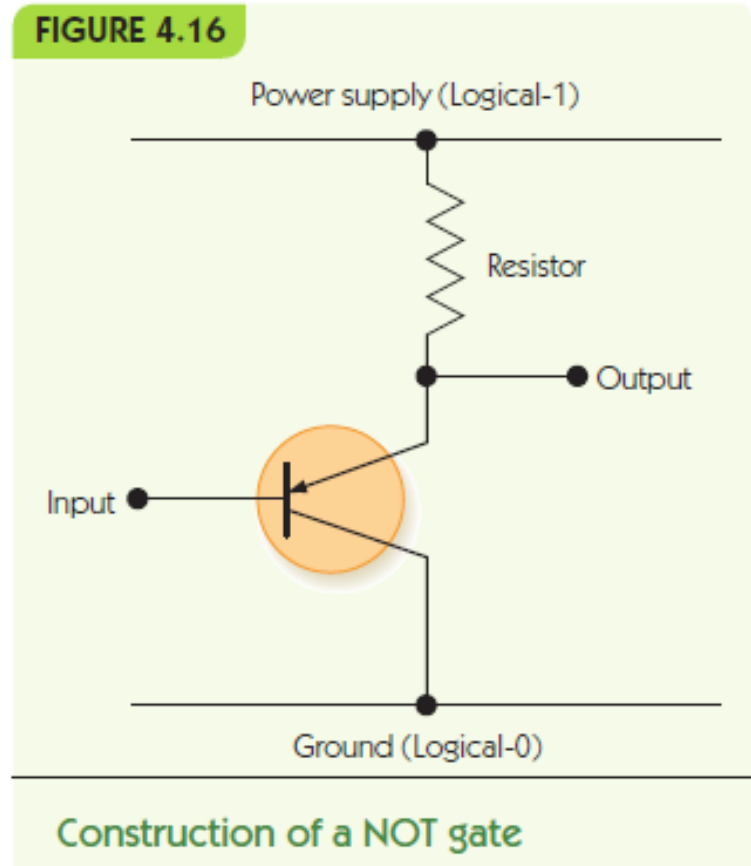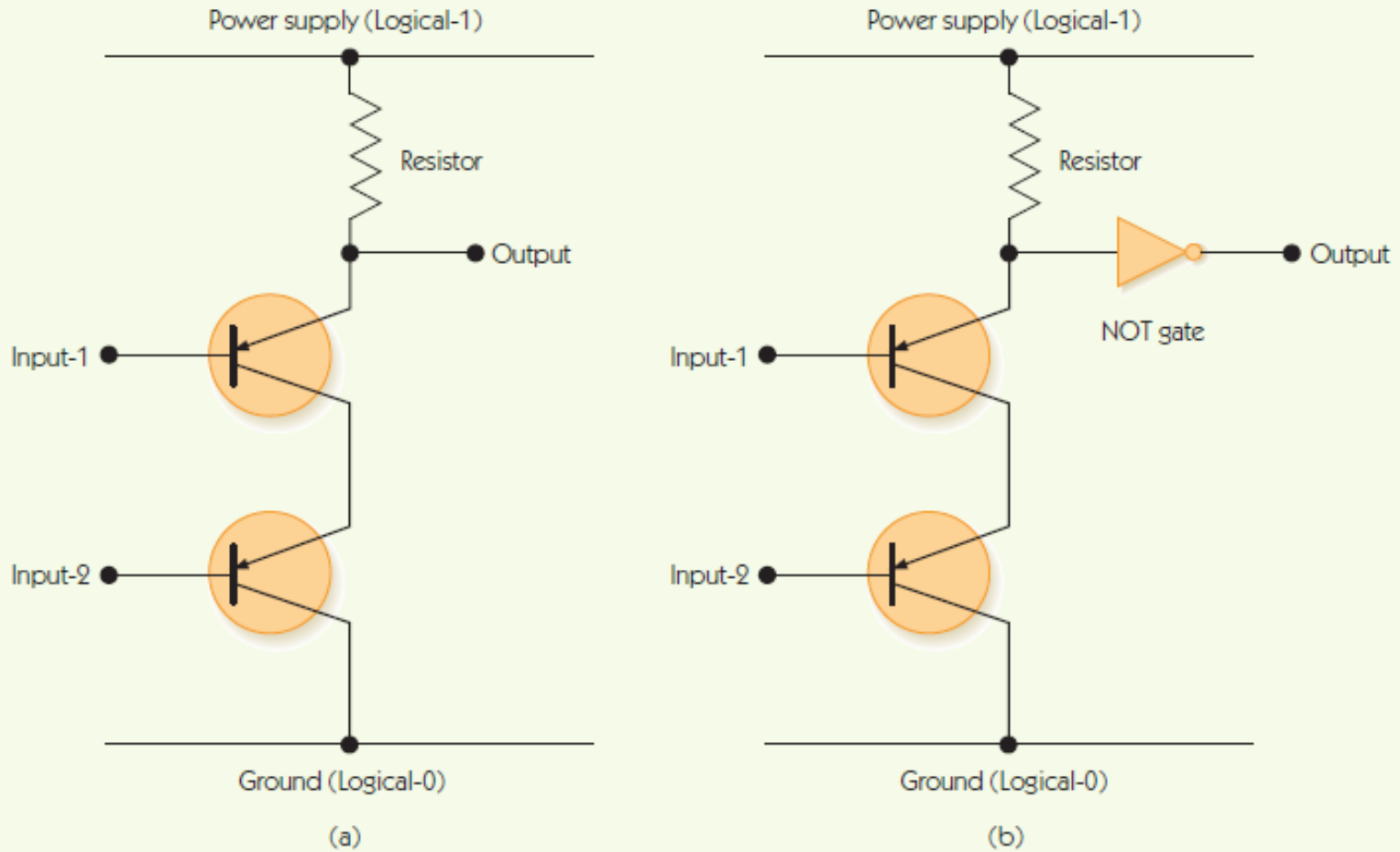

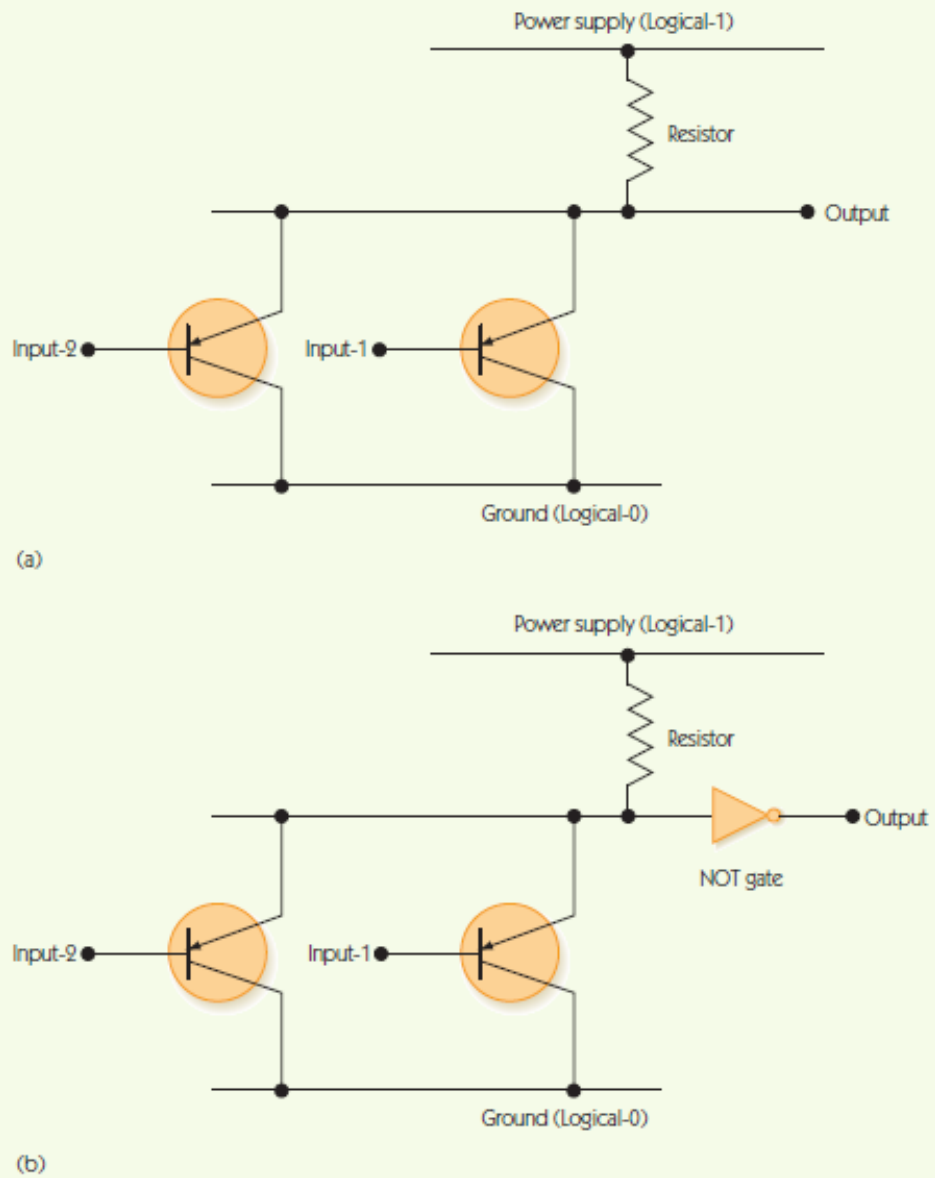


**FIGURE 4.17**



**Construction of NAND and AND gates**  
(a) A two-transistor NAND gate  
(b) A three-transistor AND gate


FIGURE 4.18



Construction of NOR and OR gates  
(a) A two-transistor NOR gate  
(b) A three-transistor OR gate
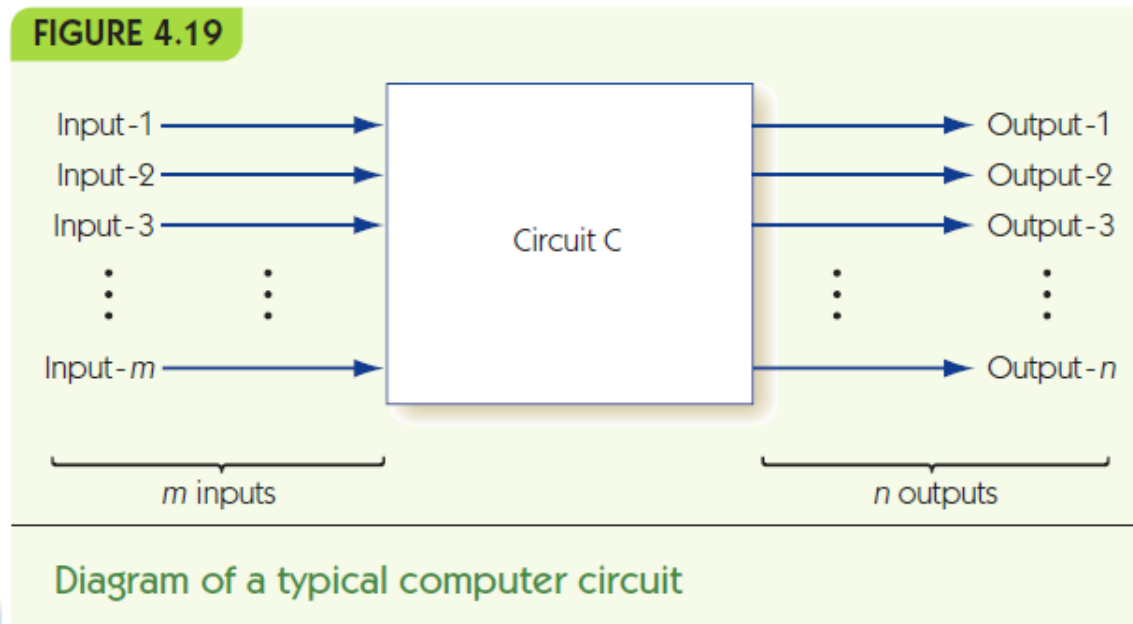
# Building Computer Circuits

- **Circuit:** has input wires, contains gates connected by wires, and has output wires
- Outputs depend only on current inputs: no state



# Building Computer Circuits (continued)

- To convert a circuit to a Boolean expression:
  - Start with output and work backwards
    - Find next gate back, convert to Boolean operator
    - Repeat for each input, filling in left and/or right side
- To convert a Boolean expression to a circuit:
  - Similar approach
- To build a circuit from desired outcomes:
  - Use standard **circuit construction algorithm**:
    - e.g., sum-of-products algorithm



# Building Computer Circuits (continued)

Example from text

- Build truth table:

| <b>a</b> | <b>b</b> | <b>c</b> | <b>Output1</b> | <b>Output2</b> |
|----------|----------|----------|----------------|----------------|
| 0        | 0        | 0        | 0              | 1              |
| 0        | 0        | 1        | 0              | 0              |
| 0        | 1        | 0        | 1              | 1              |
| 0        | 1        | 1        | 0              | 1              |
| 1        | 0        | 0        | 0              | 0              |
| 1        | 0        | 1        | 0              | 0              |
| 1        | 1        | 0        | 1              | 1              |
| 1        | 1        | 1        | 0              | 0              |

# Building Computer Circuits (continued)

Example from text

- Find true rows for Output1


| <b>a</b> | <b>b</b> | <b>c</b> | <b>Output1</b> | <b>Output2</b> |
|----------|----------|----------|----------------|----------------|
| 0        | 0        | 0        | 0              | 1              |
| 0        | 0        | 1        | 0              | 0              |
| <b>0</b> | <b>1</b> | <b>0</b> | <b>1</b>       | 1              |
| 0        | 1        | 1        | 0              | 1              |
| 1        | 0        | 0        | 0              | 0              |
| 1        | 0        | 1        | 0              | 0              |
| <b>1</b> | <b>1</b> | <b>0</b> | <b>1</b>       | 1              |
| 1        | 1        | 1        | 0              | 0              |

# Building Computer Circuits (continued)

## Example from text

- For each true row, AND inputsto make 1
  - $a = 0, b = 1, c = 0: (\sim a \cdot b \cdot \sim c)$
  - $a = 1, b = 1, c = 0: (a \cdot b \cdot \sim c)$
- Combine row subexpressions with OR
  - $(\sim a \cdot b \cdot \sim c) + (a \cdot b \cdot \sim c)$
- Build circuit from expression
- (and repeat for other output)

FIGURE 4.20

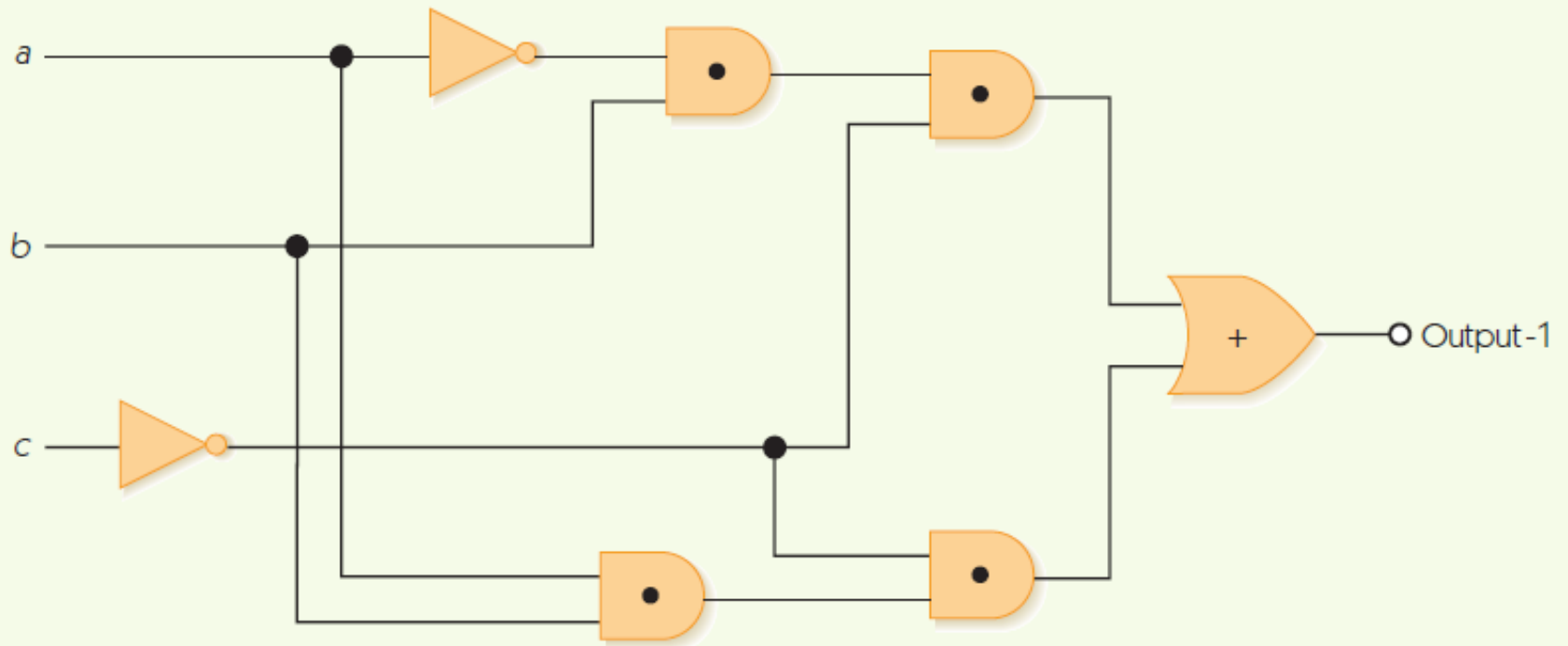

Circuit diagram for the output labeled Output-1



## FIGURE 4.21

1. Construct the truth table describing the behavior of the desired circuit
2. While there is still an output column in the truth table, do Steps 3 through 6
3.     Select an output column
4.     Subexpression construction using AND and NOT gates
5.     Subexpression combination using OR gates
6.     Circuit diagram production
7. Done

### The sum-of-products circuit construction algorithm

# Building Computer Circuits (continued)

## **Compare-for-equality (CE) circuit**

- Input is two unsigned binary numbers
- Output is 1 if inputs are identical, and 0 otherwise
- Start with one-bit version (1-CE) and build general version from that

# Building Computer Circuits (continued)


- 1-CE circuit: compare two input bits for equality
- Truth table:

| a | b | Output |
|---|---|--------|
| 0 | 0 | 1      |
| 0 | 1 | 0      |
| 1 | 0 | 0      |
| 1 | 1 | 1      |

- Boolean expression:  $(a \cdot b) + (\sim a \cdot \sim b)$

FIGURE 4.22

1-CE Circuit

 


One-bit compare-for-equality circuit



# Building Computer Circuits (continued)

- N-bit CE circuit
- Input:  $a_0a_2\dots a_{n-1}$  and  $b_0b_2\dots b_{n-1}$ , where  $a_i$  and  $b_i$  are individual bits
- Pair up corresponding bits:  $a_0$  with  $b_0$ ,  $a_1$  with  $b_1$ , etc.
- Run a 1-CE circuit on each pair
- AND the results

**FIGURE 4.23**

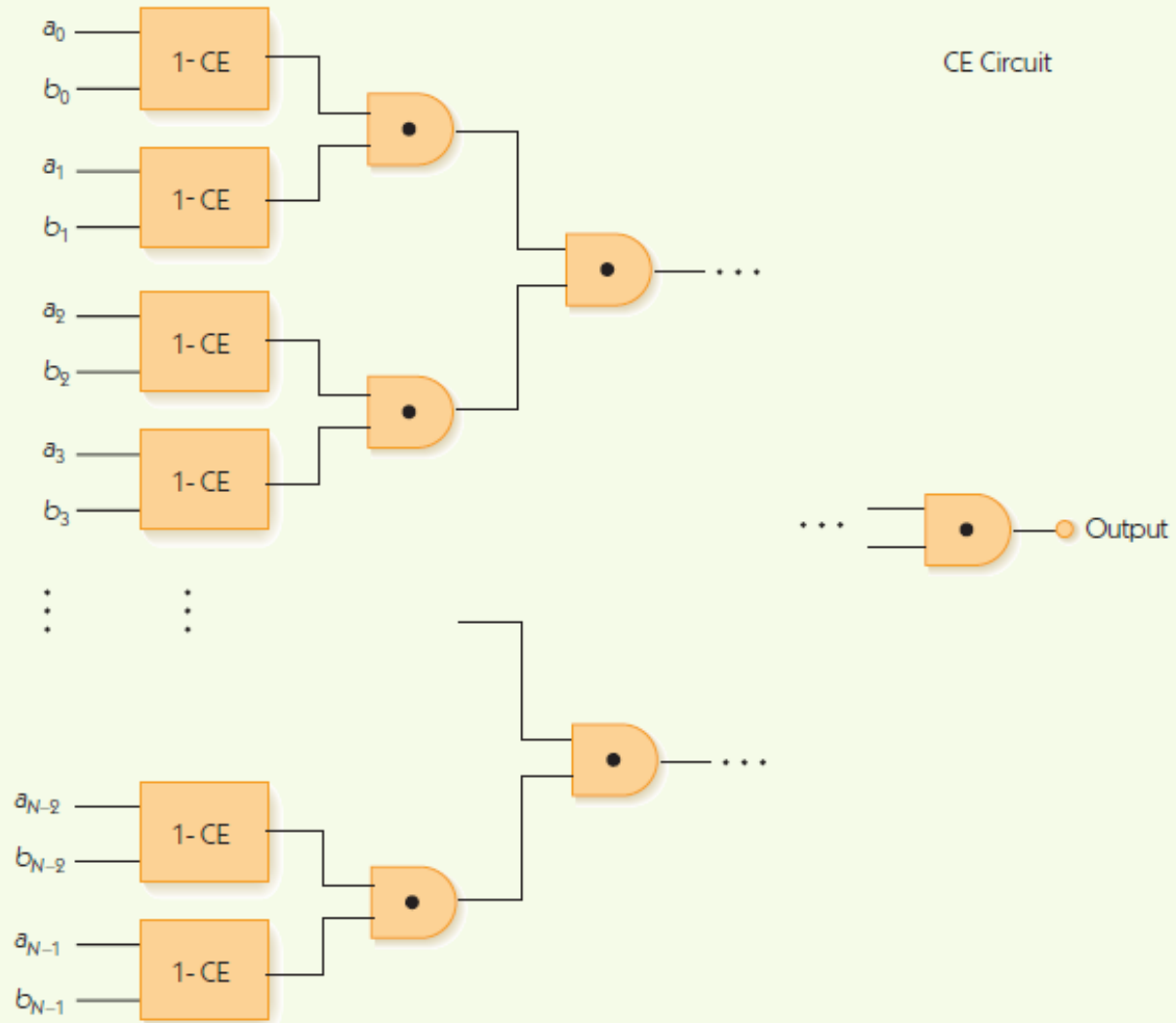

**$N$ -bit compare-for-equality circuit**

# Building Computer Circuits (continued)


## Full adder circuit

- Input is two unsigned N-bit numbers
- Output is one unsigned N-bit number, the result of adding inputs together
- Example:

$$\begin{array}{r} \phantom{+} \phantom{0} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \\ + \phantom{0} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \phantom{1} \\ \hline \phantom{0} \phantom{0} \phantom{1} \phantom{1} \phantom{1} \phantom{0} \end{array}$$

- Start with one-bit adder (1-ADD)

**FIGURE 4.24**

 

| Inputs |       |       | Outputs |           |
|--------|-------|-------|---------|-----------|
| $a_i$  | $b_i$ | $c_i$ | $s_i$   | $c_{i+1}$ |
| 0      | 0     | 0     | 0       | 0         |
| 0      | 0     | 1     | 1       | 0         |
| 0      | 1     | 0     | 1       | 0         |
| 0      | 1     | 1     | 0       | 1         |
| 1      | 0     | 0     | 1       | 0         |
| 1      | 0     | 1     | 0       | 1         |
| 1      | 1     | 0     | 0       | 1         |
| 1      | 1     | 1     | 1       | 1         |


**The 1-ADD circuit and truth table**



# Building Computer Circuits (continued)

- Sum digit,  $s_i$ , has Boolean expression:  
$$(\sim a_i \cdot \sim b_i \cdot c_i) + (\sim a_i \cdot b_i \cdot \sim c_i) +$$
$$(a_i \cdot \sim b_i \cdot \sim c_i) + (a_i \cdot b_i \cdot c_i)$$
- Carry digit,  $c_{i+1}$ , has Boolean expression:  
$$(\sim a_i \cdot b_i \cdot c_i) + (a_i \cdot \sim b_i \cdot c_i) +$$
$$(a_i \cdot b_i \cdot \sim c_i) + (a_i \cdot b_i \cdot c_i)$$


FIGURE 4.25

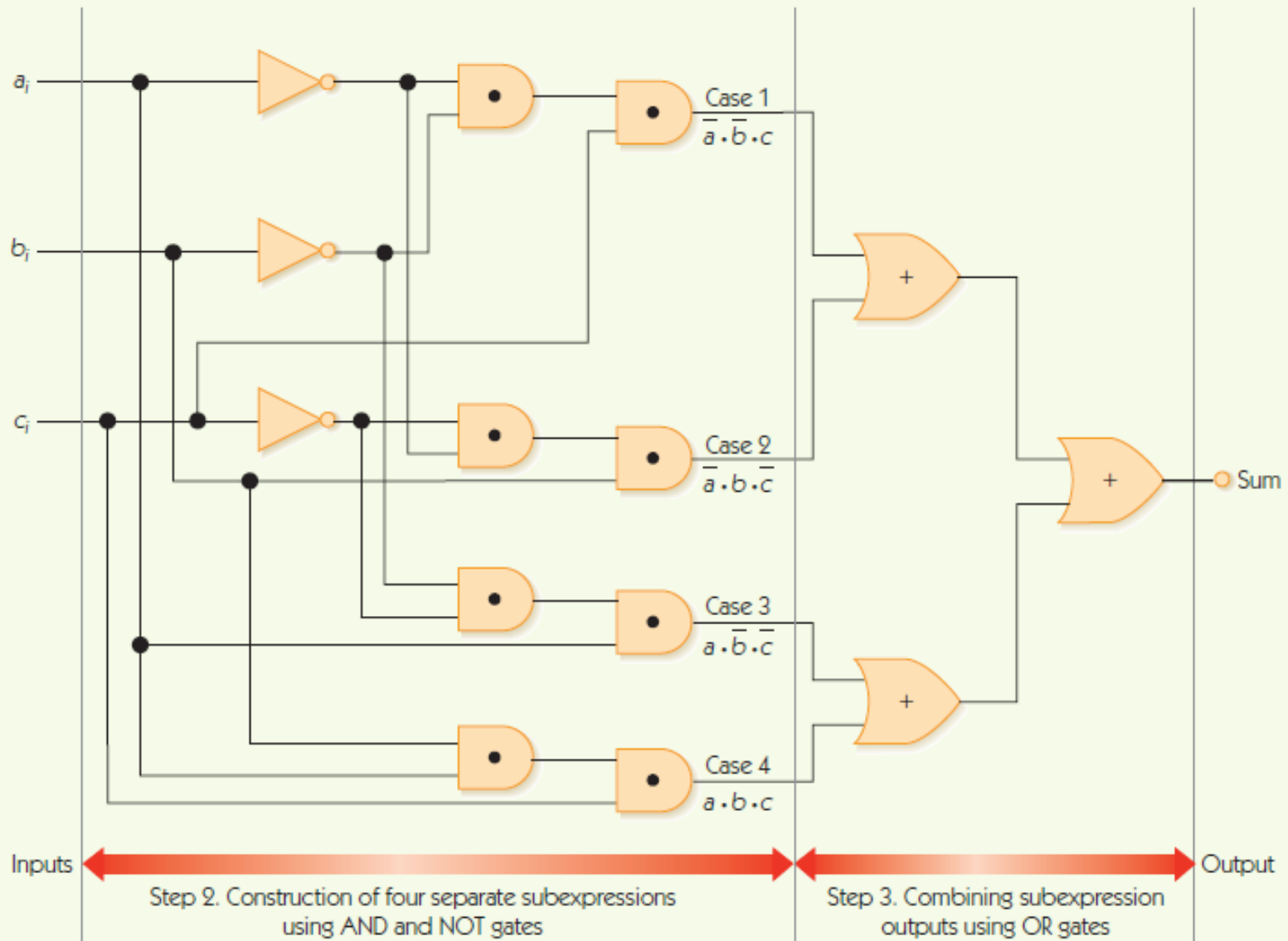

Sum output for the 1-ADD circuit

FIGURE 4.26

1 – ADD Circuit

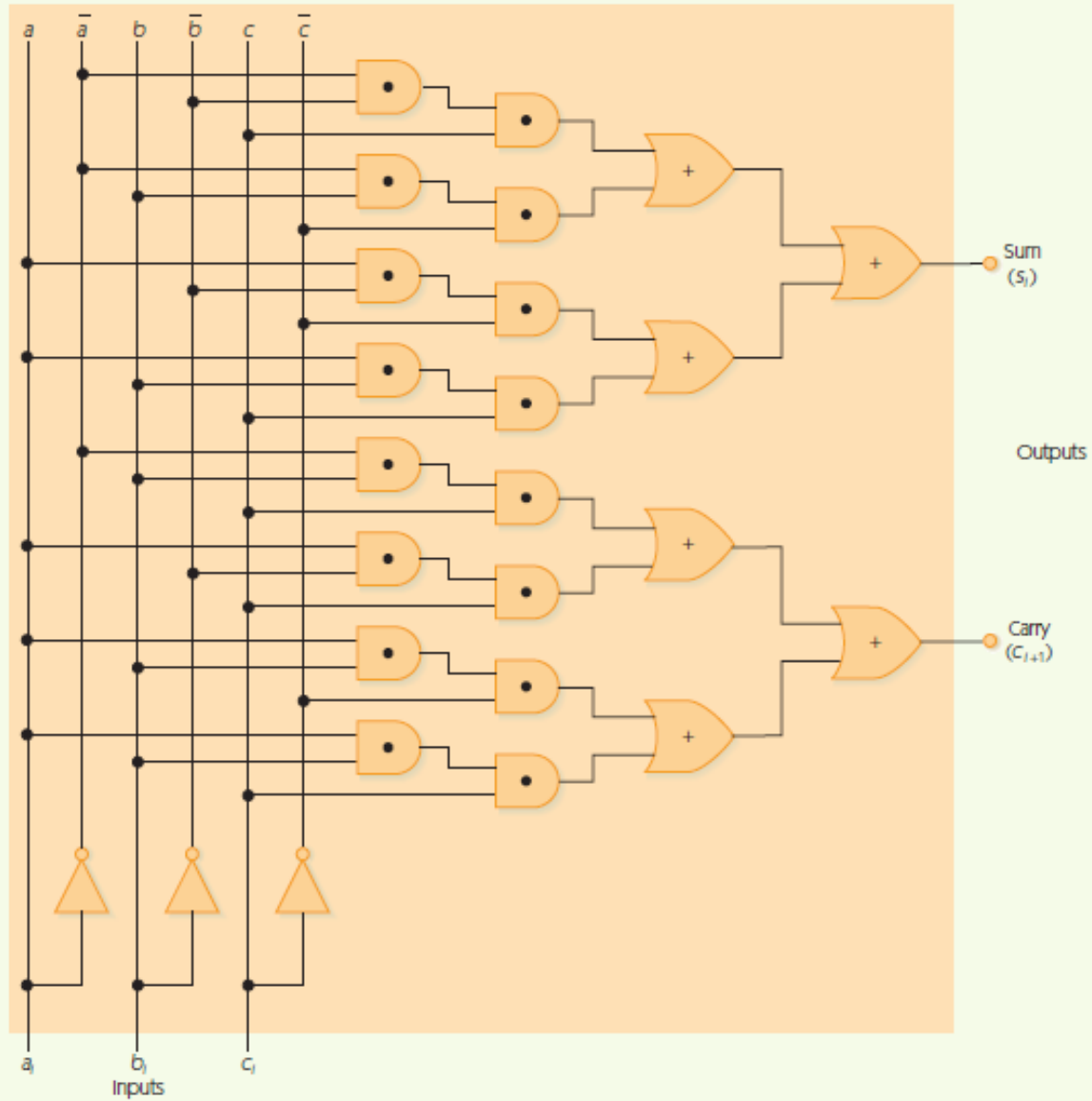


Complete 1-ADD circuit for 1-bit binary addition

# Building Computer Circuits (continued)

- N-bit adder circuit
- Input:  $a_0a_2\dots a_{n-1}$  and  $b_0b_2\dots b_{n-1}$ , where  $a_i$  and  $b_i$  are individual bits
- $a_0$  and  $b_0$  are least significant digits: ones place
- Pair up corresponding bits:  $a_0$  with  $b_0$ ,  $a_1$  with  $b_1$ , etc.
- Run 1-ADD on  $a_0$  and  $b_0$ , with fixed carry in  $c_0 = 0$
- Feed carry out  $c_1$  to next 1-ADD and repeat



**FIGURE 4.27**

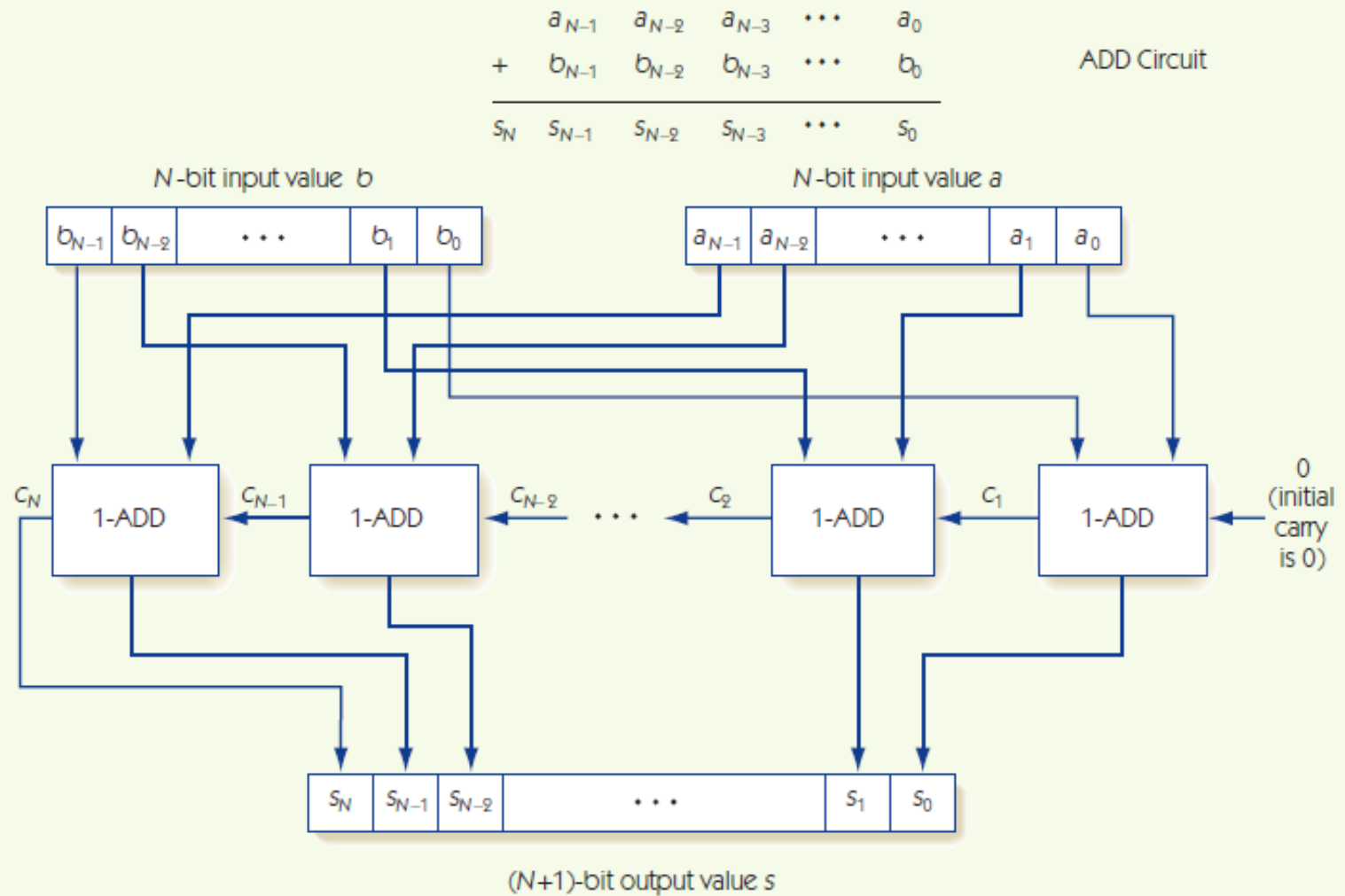


The complete full adder ADD circuit

# Control Circuits

- **Control circuits** make decisions, determine order of operations, select data values
- **Multiplexor** selects one from among many inputs
  - $2^N$  input lines
  - N selector lines
  - 1 output line
- Each input line corresponds to a unique pattern on selector lines
- That input value is passed to output

**FIGURE 4.28**

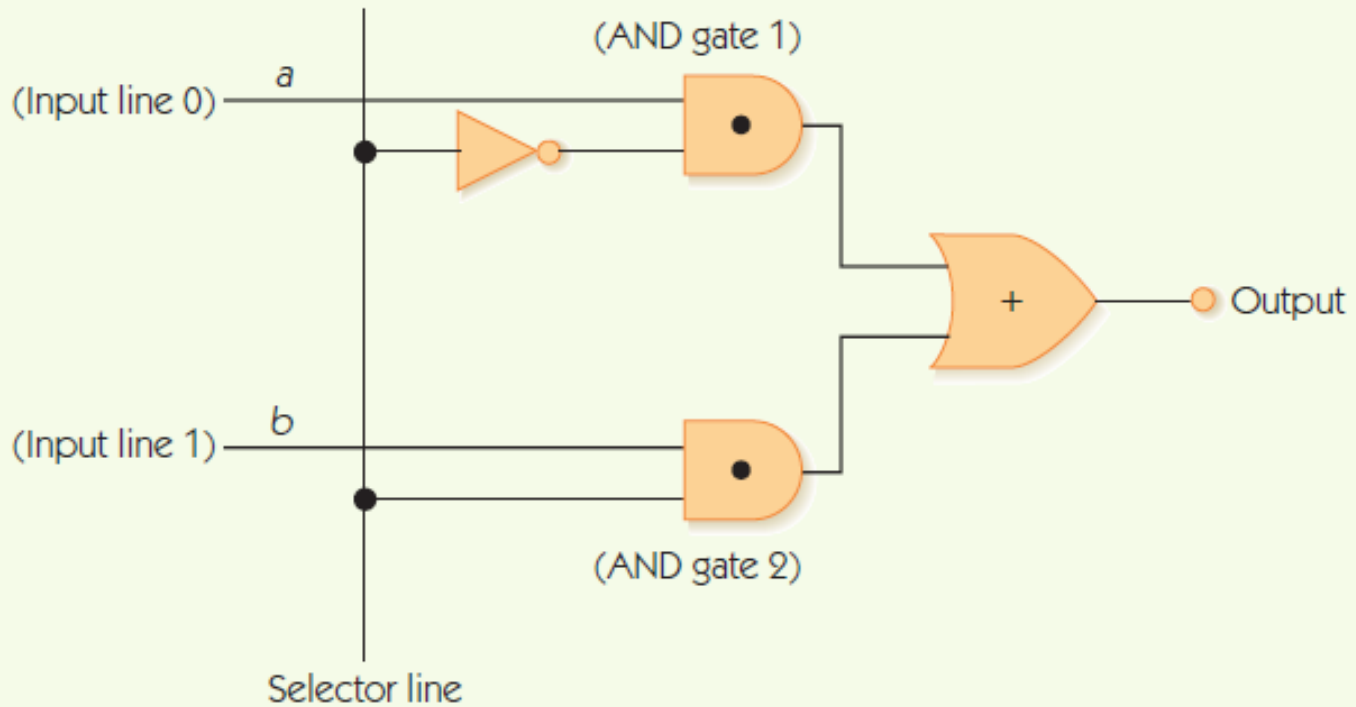


**A two-input multiplexor circuit**

# Control Circuits (continued)

- **Decoder** sends a signal out only one output, chosen by its input
  - N input lines
  - $2^N$  output lines
- Each output line corresponds to a unique pattern on input lines
- Only the chosen output line produces 1, all others output 0



FIGURE 4.29

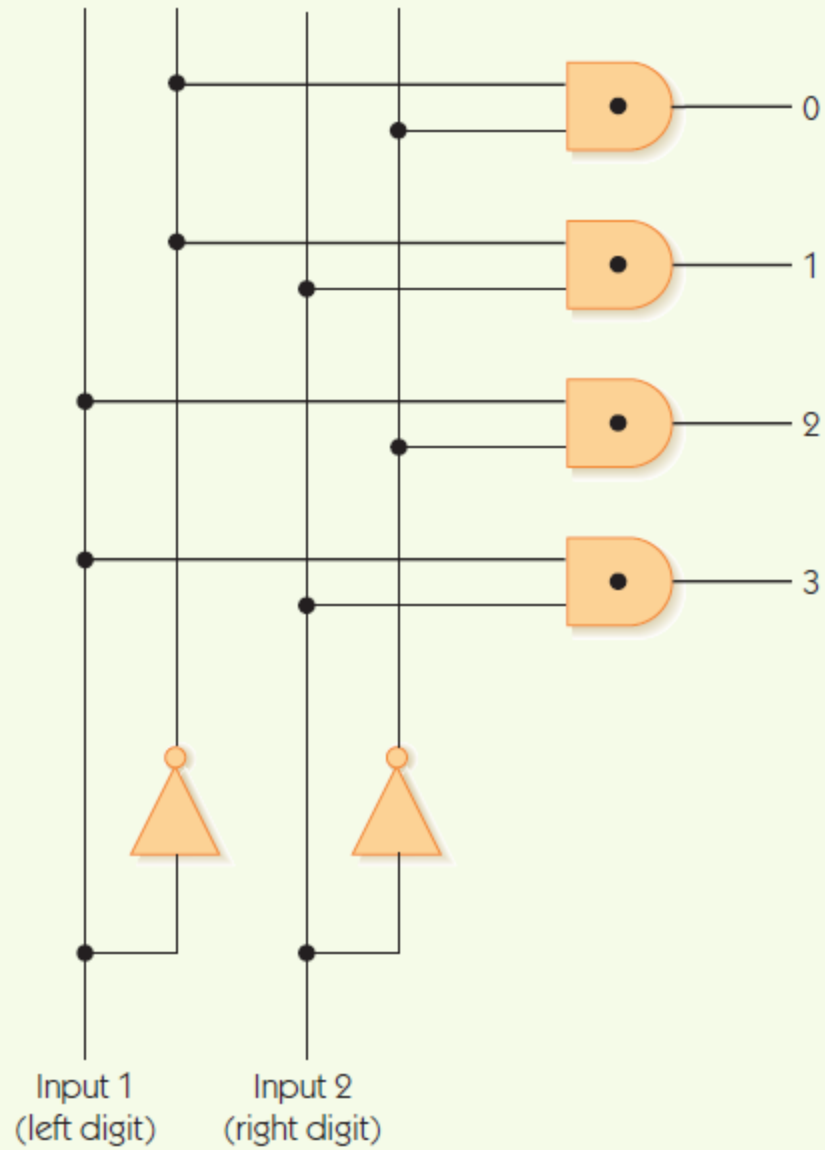


A 2-to-4 decoder circuit

# Control Circuits (continued)

- Decoder circuit uses
  - To select a single arithmetic instruction, given a code for that instruction
  - Code activates one output line, that line activates corresponding arithmetic circuit
- Multiplexor circuit uses
  - To choose one data value from among a set, based on selector pattern
  - Many data values flow into the multiplexor, only the selected one comes out


**FIGURE 4.30**

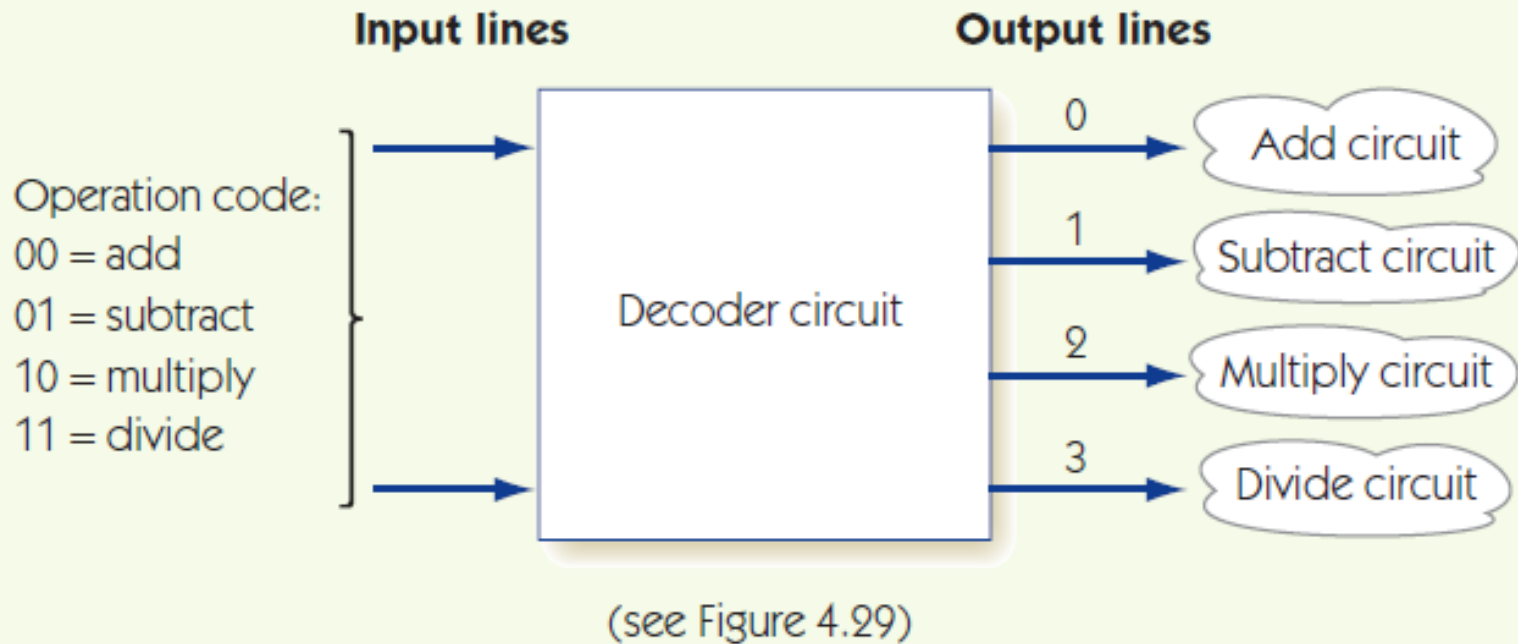

Example of the use of a decoder circuit

**FIGURE 4.31**

**Registers**

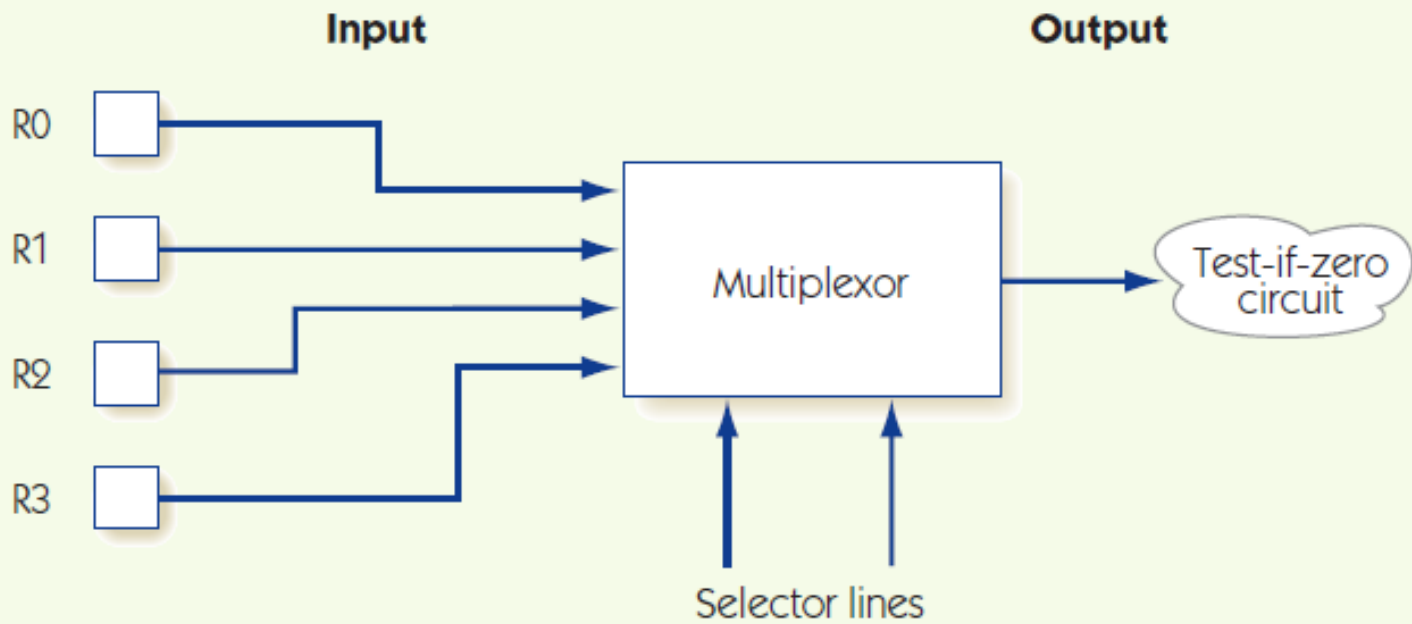

Example of the use of a multiplexor circuit



# Summary

- Computers use binary representations because they maximize reliability for electronic systems
- Many kinds of data may be represented at least in an approximate digital form using binary values
- Boolean logic describes how to build and manipulate expressions that are true/false
- We can build logic gates that act like Boolean operators using transistors
- Circuits may be built from logic gates: circuits correspond to Boolean expressions

# Summary

- Sum-of-products is a circuit design algorithm: takes a specification and ends with a circuit
- We can build circuits for basic algorithmic tasks:
  - Comparisons (compare-for-equality circuit)
  - Arithmetic (adder circuit)
  - Control (multiplexor and decoder circuits)